

93/100

**University of New Mexico**  
Department of Electrical and Computer Engineering

**ECE 321 – Electronics I (Fall 2011)**

**Exam 1**

Name: Edgar Chavez


Date: September 26, 2011

Note: Only calculator, pencils, and pens are allowed.

8

1. (10 points) True or false:

 - (a) Drain potential in PMOS is higher than the source potential. ( F ) ✓ PMOS - source = high
- (b) The width of depletion region in a PN junction increases, by decreasing the N and P doping concentration. ( T ) ✓
- (c) The diffusion current occurs because of applied electric field. ( T ) ✗ F
- (d) The change of threshold voltage due to the change in the bulk potential is called "channel length modulation". ( F ) ✓
- (e) The threshold voltage of a "depletion type" PMOS is positive. ( T ) ✓



10

2. (10 points) Consider the following logic circuit. Reduce this logic to minimum gates.


$$X + XZ + \bar{X}Y = F$$

$$X(1+Z) + \bar{X}Y = F$$

$$X + \bar{X}Y = F$$

$$(X + \bar{X})(X + Y) = F$$

$$F = X + Y$$

 

15

3. (20 points) The voltage of a forward bias diode increases by 60mV. Compute the amount of the diode current increase due to this voltage change.

Hint: Assume the diode current equation can be approximated by  $I_D \approx I_S \cdot e^{\frac{V_D}{V_{th}}}$

$$I_D \approx I_S e^{V_D/V_{TH}} \quad V_{D1} = 0 \Rightarrow I_{D1} \approx I_S$$

$$V_{D2} = 60 \text{ mV} \Rightarrow I_{D2} \approx I_S e^{60 \text{ mV}/V_{TH}}$$

$$\Delta I_D = I_{D2} - I_{D1} \approx I_S e^{60 \text{ mV}/V_{TH}} - I_S$$

$$\approx I_S (e^{60 \text{ mV}/V_{TH}} - 1)$$

if  $T = 300 \text{ K} \rightarrow V_{TH} = 26 \text{ mV}$

$$\Delta I_D \approx I_S (e^{60 \text{ mV}/26 \text{ mV}} - 1) \approx 9.05 I_S$$

20

4. (20 points) In the circuit below, assume that the depletion mode NMOS has  $K'_n = 100 \mu\text{A/V}^2$ ,  $(W/L) = 10$ , and  $V_{tn} = -1\text{V}$ . Ignore the body effect and channel length modulation.

- (a) Identify Source, Gate, and Drain terminals  
(b) Find the region of operation  
(c) Determine  $I_{DS}$

$$V_{TN} = -1 \Rightarrow |V_{TN}| = 1\text{V}$$

$$V_{GS} = 1.5 - 1.5 = 0\text{V}$$

$$V_{DS} = 2 - 1.5 = 0.5\text{V}$$

$$V_{DS} < V_{GS} - V_T$$


$$0.5 < 0 - (-1)$$

b)  $0.5 < 1 \Rightarrow \text{linearity}$

$$I_{DS} = K'_n \left(\frac{W}{L}\right) \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$


$$I_{DS} = 100 \mu\text{A/V}^2 (10) \left[ (0+1)(0.5) - \frac{(0.5)^2}{2} \right]$$

c)  $I_{DS} = 37.5 \mu\text{A}$

 

20

 
5. (20 points) Assume that the diode D1 has  $V_f = 0.7V$  and  $I_s = 1nA$  and the Zener diode Z1 has  $V_z = 6.8V$ ,  $V_f = 0.7V$ , and  $I_s = 0$ . Determine  $I_x$  and  $V_o$ .



$$I_{DZ} = I_{S2} e^{V_D/V_{TH}}$$

$$I_{DZ} = 0 (e^{V_D/V_{TH}})$$

$$I_{DZ} = 0 A$$

 

$$10V / \left(\frac{10}{15}\right) = 6.6$$

$$10V = I_x 5K + 0.7 + I_x 10K$$

$$10V = 15K I_x + 0.7$$

$$15K I_x = 9.3V$$

$$I_x = \frac{9.3}{15K} = 620 \mu A$$

$$V_o = I_x 10K$$

$$= 620 \mu A (10,000)$$

$$\approx 6.20V$$


$M=10^6$  20

6. (20 points) Analyze the circuit to determine the voltages at all nodes and the currents through all branches. Let  $V_{Tn}=1V$ ,  $K'_n=100 \mu A/V^2$ , and  $(W/L)=10$ .

$$V_G = 10 \left( \frac{10M}{10M+10M} \right) = 5V$$

$$I_{RG1} = \frac{10-5}{10M} = \frac{5}{10M} = 500nA$$
 
$$I_{RG2} = \frac{0-5}{10M} = \frac{-5}{10M} = -500nA$$



$$V_1 = I_{DS} (6k)$$

Assume saturation:  $V_{DS} > V_{GS} - V_{Tn}$

$$I_{DS} = \frac{K'_n}{2} \left( \frac{W}{L} \right) (V_{GS} - V_{Tn})^2$$

$$V_{GS} = V_G - V_1$$

$$V_{DS} = V_O - V_1$$

$$= 5 - I_{DS} (6k)$$

$$I_{DS} = \frac{100 \mu A/V^2}{2} (10) (5 - I_{DS} (6k) - 1)^2$$


$$I_{DS} = 500 \mu A \quad \text{or} \quad I_{DS} = 888 \mu A$$

$$\text{IF } I_{DS} = 500 \mu A \rightarrow V_1 = 500 \mu A (6k) = 3 \Rightarrow V_{GS} = 5 - 3 = 2V \Rightarrow V_O = 7V$$

$$\text{IF } I_{DS} = 888 \mu A \rightarrow V_1 = 888 \mu A (6k) = 4.8 \Rightarrow V_{GS} = 5 - 4.8 = 0.2V \Rightarrow V_O = 5V$$

$$I_{DS} = 888 \mu A \rightarrow V_{GS} = 0.2V < V_{Tn}$$
 
$$I_{DS} = 500 \mu A \quad V_O = 7V \quad V_1 = 3V$$



University of New Mexico  
Department of Electrical and Computer Engineering

ECE 321 – Electronics I (Fall 2011)

Exam 2

Name: Edgar Chavez

Date: Nov. 16, 2011

Note: Only calculator, pencils, and pens are allowed.



10

1. (10 points) True or false:



- (a) Higher noise margin is always desirable. ( T ) ✓
- (b) To decrease  $t_{pHL}$ , the NMOS threshold voltage must be increases. ( F ) ✓
- (c) When the input of a CMOS inverter is high, the leakage current will be determined by  $I_{OFF}$  of PMOS. ( T ) ✓
- (d) In a CMOS inverter, the faster input rise time results in higher short-circuit power. ( F ) ✓
- (e) The propagation delay in a simple RC network is 0.69 times of its time-constant. ( T ) ✓

15

  2. (15 points) Given the delay of a standard fanout-4 delay is 50ps (i.e. 1x inverter driving a 4x inverter), determine the delay in each of the following cases:




$n \propto t_p$

  



2

 3. (10 points) Determine the  $(W/L)_p$  of the PMOS transistor in a CMOS inverter such that the switching threshold voltage,  $V_M$ , becomes exactly  $V_{DD}/2$ . Assume that  $K'_n = 120 \mu A/V^2$ ,  $V_{tn} = 0.3V$ ,  $\lambda_n = 0.01V^{-1}$ ,  $(W/L)_n = 10$ ,  $K'_p = 50 \mu A/V^2$ ,  $V_{tp} = -0.4V$ ,  $\lambda_p = -0.02V^{-1}$  and  $V_{DD} = 1.2V$ . Include the channel length modulation effect into your calculation.



Assume saturation:

$$|I_{DS}| = \frac{K'_p}{2} \left(\frac{W}{L}\right)_p (V_{GS} - |V_{TP}|)^2 = \frac{50 \mu A/V^2}{2} \left(\frac{W}{L}\right)_p (V_M - 0.4)^2$$

Since  $(\frac{W}{L})_n = 10$  then  $(\frac{W}{L})_p \approx 2 \left(\frac{W}{L}\right)_n = 20$

2

4. (10 points) Calculate the short circuit current,  $I_{DDMax}$ , in the CMOS inverter of problem 3. Again, include the channel length modulation effect into your calculation.

$$I_{DDMax} = I_{SC} = I_{av} \cdot V_{DD} = P_{SC}$$

$$I_{av} = 462 \mu A$$

$$= 554 \mu A$$


5. (10 points) The output of the CMOS inverter in problem 3 is connected to a novel Carbon Nanotube-based logic gate with  $V_{IL}=0.3V$ , and  $V_{IH}=0.8V$ . Sketch the noise margin rectangles and determine the low and high noise margin.

$$NM_H = V_{OH} - V_{IH}$$


$$NM_L = V_{IL} - V_{OL}$$

$$1.2 - 0.8 = 0.4$$

$$= 0.3 - 0 = 0.3$$

 

 6. (15 points) The output of the CMOS inverter in problem 3 is connected to a 100fF load capacitor. Use the average current technique to find high-to-low propagation delay,  $t_{PHL}$ . Include the channel length modulation effect only in saturation region, not in linear region.



$$t_{PHL} = \frac{C_L (V_{DD}/2)}{I_{av}}$$

PMOS: OFF

NMOS: ON

$V_{GS} = 1.2$   $V_{DS} = V_{DD} = 1.2 \Rightarrow$  saturation

$$(A) \quad I_{DS1} = \frac{k'_n (W/L)_n}{2} (V_{GS} - V_{Tn})^2 (1 + \lambda_n V_{DS})$$

$$= \frac{120 \mu A}{2} (10) (1.2 - 0.3)^2 (1 + 0.01(1.2)) = 492 \mu A$$

$$(B) \quad V_{GS} = 1.2 \quad V_{DS} = V_{DD}/2 = 0.6 \Rightarrow \text{linear}$$

$$I_{DS2} = k'_n (W/L)_n \left[ (V_{GS} - V_{Tn}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$= 120 \mu A (10) \left[ (1.2 - 0.3)(0.6) - \frac{(0.6)^2}{2} \right] = 432 \mu A$$

$$I_{av} = \frac{492 \mu A + 432 \mu A}{2} = 462 \mu A$$

$$t_{PHL} = \frac{(100 \text{ fF})(1.2/2)}{462 \mu A} = 129.87 \text{ ps}$$

- 10 7. (10 points) Determine the dynamic power consumption in the CMOS inverter of problem 6, if a square wave pulse running at 1GHz frequency is applied to its input.

$$\begin{aligned}\text{Dynamic Power} &= V_{DD}^2 C_L f \\ &= (1.2)^2 (100 \text{ fF}) (1 \text{ GHz}) \\ &= 144 \mu\text{W}\end{aligned}$$

- 10 8. (10 points) Calculate the equivalent output resistance,  $R_{OHL}$ , of the inverter in problem 3 for the high-to-low transition. Use the results that you found in problem 6.

$$R_{OHL} = \frac{V_{DD}/2}{0.69 I_{av}} = \frac{1.2/2}{0.69 I_{av}}$$

$$I_{av} \text{ from problem 6} = 462 \mu\text{A}$$


$$R_{OHL} = \frac{0.6}{0.69 (462 \mu\text{A})} = 1,882.18 \Omega$$



10

9. (10 points) The CMOS inverter of problem 3 is connected to an interconnect network shown below. Use the  $R_{oHL}$  found in problem 8 to find the high-to-low propagation delay,  $t_{PHL}$ .

$$t_{PHL} = 0.69\tau$$

 

$$\begin{aligned}\tau &= 20\text{fF}(2\text{k} + 1882.18) + 10\text{fF}(3\text{k} + 1882.18) + 30\text{fF}(5\text{k} + 1882.18) \\ &\quad + 30\text{fF}(2\text{k} + 1882.18) + 20\text{fF}(2\text{k} + 1882.18) \\ &\quad + 20\text{fF}(3\text{k} + 1882.18) \\ &= 624.68\text{ps}\end{aligned}$$

$$\begin{aligned}t_{PHL} &= 0.69(624.68\text{ps}) \\ &= 431.03\text{ps}\end{aligned}$$