

University of New Mexico
Department of Electrical and Computer Engineering

ECE 321 – Electronics I (Fall 2018)


Exam #2

Name: _____

Date: Nov. 5, 2018

Note: Only calculator, pencils, and pens are allowed.

 
1. (10 points) Fill in the blank:
 - (a) To decrease t_{pHL} , the NMOS threshold voltage must be _____.
 - (b) A 10% reduction in power supply voltage reduces the dynamic power dissipation by _____.
 - (c) By definition rise time is the time it takes for the output to go from _____ to _____.
 - (d) The propagation delay in an RC circuit, when $R=15\text{K}\Omega$ and $C=12\text{PF}$ is _____.
 - (e) The dynamic power of an inverter driving a 10PF capacitor at 1GHz when $V_{DD}=3.3\text{V}$ is _____.
2. (15 points) For the following NMOS circuit, find V_{out} . Assume that $K'_n=100\mu\text{A}/\text{V}^2$, $(W/L)=5$, $V_T=0.8\text{V}$, and $\lambda=0$.



3. (15 points) We would like to design a CMOS inverter such that the switching threshold voltage, V_M , becomes $V_{DD}/2$. Determine the (W/L) ratio of PMOS if the (W/L) ratio of NMOS is 10. Let $V_{DD}=5V$, $V_{Tn}=1.2V$, $K'_n=100 \mu A/V^2$, $\lambda_n=0.1 V^{-1}$, $V_{Tp}=-1V$, $K'_p=60 \mu A/V^2$, $\lambda_p=0.2 V^{-1}$. Include the channel length modulation effect into your calculations.
4. (10 points) Determine the peak power supply current, I_{DDMax} , of the inverter that you designed in Problem 3.

5. (20 points) The slope of the VTC of a CMOS inverter is $g=12$ and its switching threshold voltage, V_M , is 1.5V. If $V_{DD}=3.3V$, determine V_{OH} , V_{OL} , V_{IL} , V_{IH} , NMH , and NML of this inverter.

 6. (15 points) Assume that the voltage of all nodes in the following circuit start at 0V. Determine the final voltage of nodes V_1 , V_2 , V_3 , and V_4 . Let $V_{tn}=0.8V$ and ignore body effect.



7. (15 points) We would like to design a CMOS inverter such that it gives a symmetric rise and fall propagation delay, *i.e.* $t_{PHL} = t_{PLH}$. Determine the (W/L) ratio of the PMOS if (W/L) ratio of the NMOS is 10. Let $V_{DD} = 5V$, $V_{Tn} = 1.2V$, $K'_n = 100 \mu A/V^2$, $\lambda_n = 0.1 V^{-1}$, $V_{Tp} = -1V$, $K'_p = 60 \mu A/V^2$, $\lambda_p = -0.2 V^{-1}$. Include the channel length modulation effect into your calculations for saturation current only.

Hint: You don't need the value of the load capacitance, C_L , to solve this problem.