

University of New Mexico
Department of Electrical and Computer Engineering

ECE 321 – Electronics I (Fall 2018)

Final Exam

Name: _____


Date: Dec. 10, 2018

Note: Only calculator, pencils, and pens are allowed.


1. (10 points) True or false:
- (a) A diode is forward bias if its current flows from Anode to Cathode. ()
 - (b) A bridge rectifier is a half-wave rectifier that contains four diodes. ()
 - (c) In a PMOS the Drain has higher potential than the Source. ()
 - (d) Due to DIBL effect, increasing the Drain voltage results in an increase in threshold voltage of an NMOS. ()
 - (e) Because of the threshold voltage roll-off, the threshold voltage of a long channel NMOS is higher than that of shorter channel NMOS. ()
 - (f) The fanout of a 2X inverter driving two 1X inverters is 1. ()
 - (g) Setup time is the amount of time that the data must be stable after the rising edge of the clock. ()
 - (h) Hot electrons are the high energy electrons that get stuck into the gate oxide close to the Source side. ()
 - (i) The longest path in a VLSI circuit is called critical path. ()
 - (j) The hold time constraint in a digital system can be relaxed by reducing the clock frequency. ()

 2. (5 points) Draw the logic gate implementation of an AOI gate, using NAND gates only.


Hint: Start with the circuit diagram below and convert all gates to NAND gates.



 
3. (10 points) In the circuit configuration below:
- Identify Drain and Source terminals assuming that the device is a PMOS.
 - Identify the region of operation for the PMOS.
 - Determine the drain current if $V_{Tp} = -0.4\text{V}$, $K'_p = -65\mu\text{A/V}^2$, $(W/L) = 20$, and $\lambda_p = -0.2\text{V}^{-1}$.



 
4. (10 points) The following RC network is the equivalent circuit of an interconnect network in a VLSI chip. Using Elmore delay, compute the **propagation delay** from V_{in} to V_{out} .



 
5. (10 points) Consider the given pull-down network for a complex CMOS gate shown below.
- Draw the dual pull up network.
 - Write the Boolean function representing the gate.
 - Size all transistors so that it has the same delay of a standard inverter (i.e. 1X NMOS and 2X PMOS).



 6. (10 points) In the following circuit, find V_{out} . Assume that $(W/L)_n=20$, $V_{DD}=5\text{ V}$, $K'_n=100\text{ }\mu\text{A/V}^2$, $V_{tn}=0.5\text{ V}$.




 7. (10 points) Determine the switching threshold voltage, V_M , of the three input NAND gate when all the inputs are tied together. Assume that $(W/L)_n=15$, $(W/L)_p=10$, $V_{DD}=1.2$ V, $K'_n=95$ $\mu\text{A}/\text{V}^2$, $V_{tn}=0.3$ V, $K'_p=50$ $\mu\text{A}/\text{V}^2$, and $V_{tp}=-0.4$ V in the 100nm technology node.




8. (5 points) Determine the maximum I_{DD} current for the three input NAND gate of problem 7.

 
9. (10 points) Find the current of the Zener diode, I_z , in the following circuit.
Hint: Assume that the Zener diode is in breakdown condition.



 10. (10 points) The layout of a logic gate is shown below.
- Draw the transistor schematic.
 - What logic function does this perform?
 - This layout is not complete. What is missing in this layout?



 11. (10 points) Consider the following sequential circuit with 3 edge-triggered flip-flops and logic blocks A, B, and C. Assume that $t_{SU} = 3\text{ns}$, $t_{hold} = 4\text{ns}$, and $t_{C2Q} = 2\text{ns}$.
- Identify all possible paths from Q to D of any flip-flop in this circuit. For logic block A, assume that the delay is the same for both inputs.
 - If $T_{Logic,A} = 3\text{ns}$, $T_{Logic,B} = 4\text{ns}$, and $T_{Logic,C} = 3\text{ns}$, identify the longest and the shortest path delays.
 - What is the maximum clock frequency at which the circuit can operate correctly?
 - Does this circuit satisfy the hold time constraint? Why?



12. (5 bonus points) In this course, you have spent several hours to design the layout of a 2-input multiplexer from scratch. Give 3 important things that you learned by working on this project.